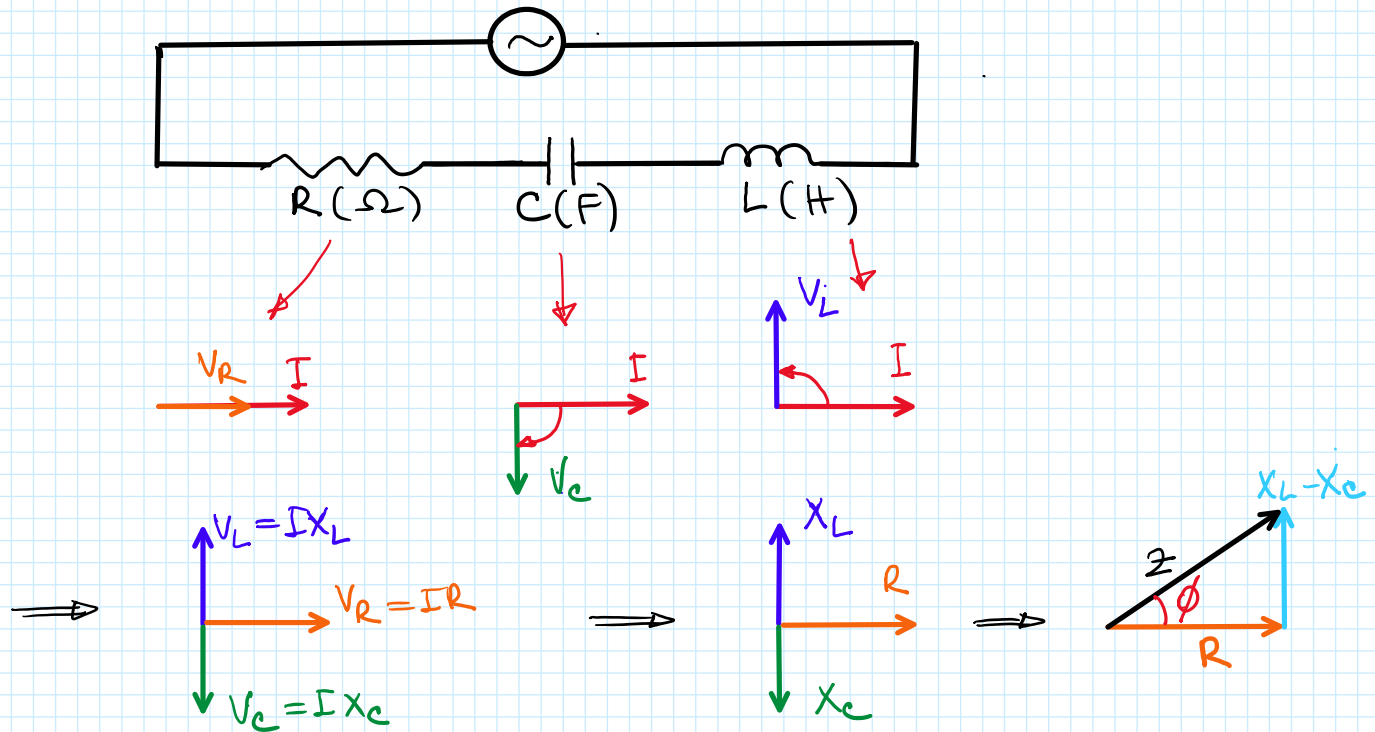


AC Circuits

→ we explore steady state AC circuits that involve inductors, capacitors, and resistors.




$$Z = R + j(X_L - X_C)$$

impedance (Ω)

ϕ - phase angle

Resistor (only)

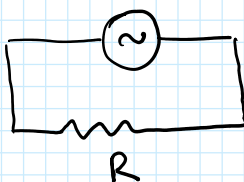


$$Z = R (\Omega)$$

→ resistance does not change with f .




→ resistance does not change with f .
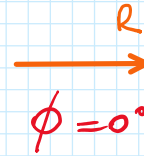
$$V_R = (I \angle 0^\circ)R = IR \angle 0^\circ$$



Inductors (only)

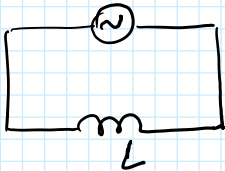


$$Z_L = j(X_L) = +j(\omega L) = j(2\pi fL)$$

$X_L = \omega L$ inductive reactance (Ω)

L - inductance (H)

→ as f increases, X_L increases

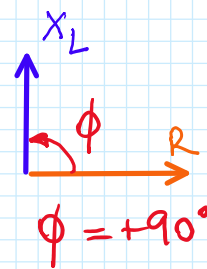


$$X_L = 2\pi fL$$

→ at extremely low frequencies $X_L \rightarrow 0$ (inductor behaves like a short) and at high frequencies, the inductor behaves like an open, $X_L \rightarrow \infty$

$$V_L = (I \angle 0^\circ)(X_L \angle 90^\circ) = IX_L \angle 90^\circ$$

$\left\{ \begin{array}{l} ELI - E \text{ leads } I \text{ in } L \text{ (inductors)} \\ VIL - V \text{ leads } I \text{ in } L \text{ (inductors)} \end{array} \right.$

Capacitors (only)

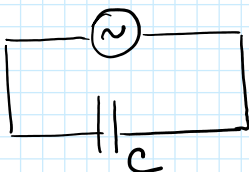


$$Z = -j(X_C) = -j\left(\frac{1}{\omega C}\right) = -j\left(\frac{1}{2\pi fC}\right)$$

$$\frac{1}{X_C} = \omega C = 2\pi f C$$

$$X_C = \frac{1}{\omega C} \quad \text{capacitive reactance } (\Omega)$$

C - capacitance (F)

→ as f increases, X_C decreases

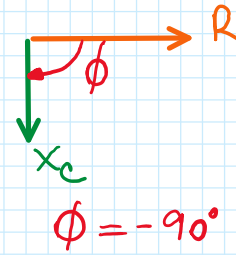

→ at extremely low frequencies $X_C \rightarrow \infty$ (the capacitor behaves like an open) and at high frequencies, the capacitor behaves like a short, $X_C \rightarrow 0$

$$V_C = (1 \angle 0^\circ)(X_C \angle -90^\circ) = IX_C \angle -90^\circ$$

ICE - I leads E in C (capacitors)

CIV - I leads V in C (capacitors)

Circuit Phase Angle

→ circuit angle is the angle between the generator voltage and generator current. We normally use the current phase angle as the reference. Assume that the source current has a phase angle of zero.

→ phase angle is positive if the voltage leads the current (the circuit has more inductive reactance than capacitive reactance).

→ phase angle is negative if the voltage lags the current (the circuit has more capacitive reactance than inductive reactance).

ELI the ICE man and CIVIL