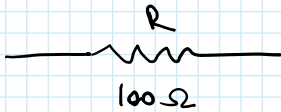


Parallel AC Circuits

→ we introduce conductance G , susceptance B , and admittance Y .


- $G = \frac{1}{R}$ conductance, in Siemens (S)

Ex: Calculate G .




- $B_L = \frac{1}{X_L}$ inductive susceptance, in Siemens (S)

Ex: Calculate B .

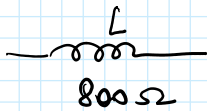


- $B_C = \frac{1}{X_C}$ capacitive susceptance, in Siemens (S)

Ex: Calculate B .

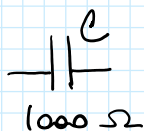

- $Y = G + j(B_C - B_L) = \frac{1}{Z}$, in Siemens (S)

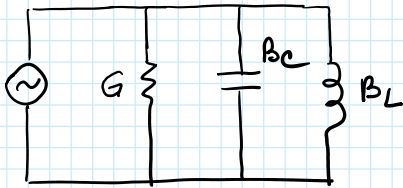Ex: Calculate Y for the circuit below. Use the previous components.



Power in AC Circuits

- **Case 1 – Purely Resistive Circuits**

- In a circuit that only contains **only** resistive components, the dissipated power is found using the same relations we used explored earlier in this course:

$$P_{Ave} = I_{RMS} V_{RMS}$$

$$P_{Ave} = I_{RMS}^2 R$$

$$P_{Ave} = \frac{V_{RMS}^2}{R}$$

- **Case 2 – RC, RL, and RLC Circuits**

- Recall that reactive components (capacitors, and inductors) do not dissipate power like resistors do, but rather they only store energy and release energy again
- In a circuit that contains a combination of resistance and reactive components, power is **only dissipated by the resistive component**

$$P_{Ave} = I_{RMS} V_{RMS} (\cos \theta)$$


Where (θ) is the circuit angle

- The expression power can also be written in a form that is common to the electrical power industry

$$P_{Ave} = I_{RMS} V_{RMS} (pf)$$

Where (pf) is the power factor equal to $\cos \theta$

Resistors in Parallel

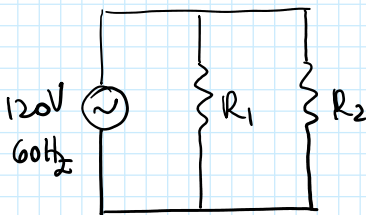

$$R_1 = 40 \Omega$$

$$R_2 = 30 \Omega$$


a) R_T , G_T

b) Z_T

c) I_T

d) phasor diagram

Inductors in Parallel

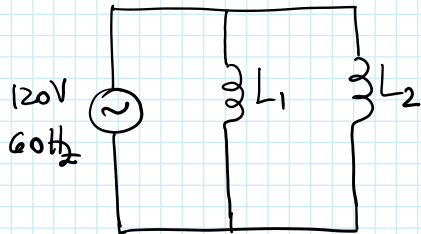


$$L_1 = 0.2 \text{ H}$$

$$L_2 = 0.5 \text{ H}$$


- a) L_T
- b) X_{LT} , B_T
- c) Z_T
- d) I_T
- e) phasor diagram

Capacitors in Parallel

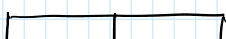

$$C_1 = 8.0 \mu\text{F}$$

$$C_2 = 2.0 \mu\text{F}$$

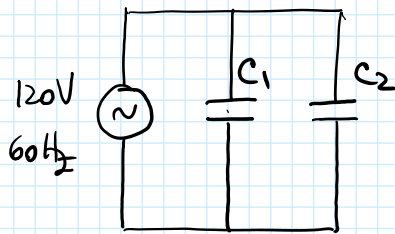


$$C_1 = 8.0 \mu F$$

$$C_2 = 22 \mu F$$


- C_T , B_T
- Z_T
- I_T
- phasor diagram

RL Circuit

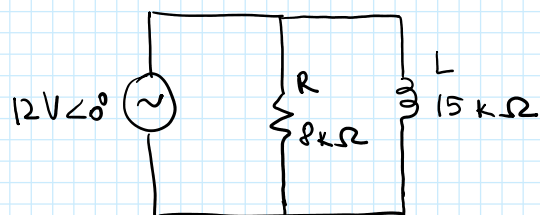


- voltages V_R, V_L
- currents I_R, I_L, I_T
- phasor diagram
- circuit phase

RC Circuit

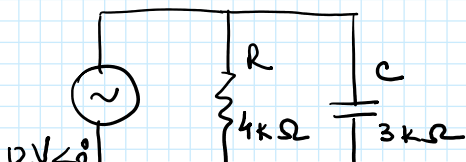

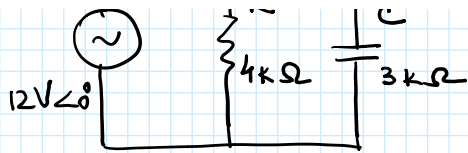
- a) voltages V_s, V_R, V_C
- b) currents I_R, I_C, I_T
- c) phasor diagram
- d) circuit phase



c) phasor diagram

d) circuit phase

RLC Circuit

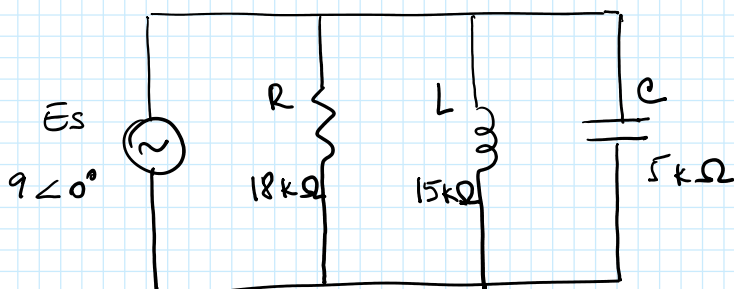

a) voltages

b) currents

c) phasor diagram

d) admittance diagram

e) circuit phase