

## Step Response of 1st Order (RC and RL circuits)

- Capacitors and inductors are energy storage elements, and they do not dissipate energy
  - Capacitors store energy as electric fields (accumulated charge)
  - Inductors store energy as magnetic fields (moving charge, or current)
  - Stored energy must be released later, but not converted to heat as resistors
    - Power relations ( $P = VI$ ,  $P = V^2/R$ , and  $P = I^2R$ ) do not apply to inductors and capacitors *it does, with 2!*
- Capacitors and inductors have nonlinear voltage-current relationships, and these quantities change with time due to storage and release of energy
  - They do ~~not~~ obey Ohm's Law *they do!*
  - Current and voltage change over time, until fully charged or discharged

### First Order Circuits

- The term first order is used to describe circuits that contain only one storage element
- Recalling that inductors and capacitors do not dissipate energy but rather temporarily store and then release their stored energy, any circuit that contains only one inductor or capacitor is considered a first order circuit
- It is assumed that the storage element is ideal (has no parasitic traits) and therefore does not have a stray resistance that would otherwise cause it to dissipate energy

→ in terms of behavior, inductors oppose to any change in current by producing a voltage, while capacitors oppose a change in voltage by producing a current.

→ for an inductor, the voltage is proportional to the rate of change in current, and the inductance.

$$v_L(t) = L \frac{\Delta i_L}{\Delta t}$$

→ for a capacitor, the current is proportional to the rate of change in voltage, and the capacitance.


$$i_C(t) = C \frac{\Delta v_C}{\Delta t}$$

→ inductors and capacitors are in steady state when their current and voltage are not changing (they are either fully charged or discharged).

$$\frac{\Delta v_C}{\Delta t} = 0 \qquad \frac{\Delta i_L}{\Delta t} = 0$$

→ when not in steady state, they either store or release energy. This corresponds to the transient period.

### Series RC Circuit Step Response

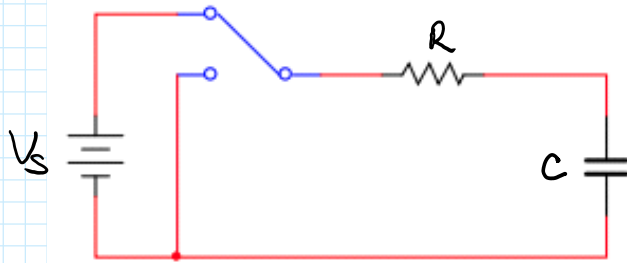

→ consider initially the capacitor not charged. When the switch is in upper position, current goes through the resistor and the capacitor gets fully charged – this is transient state. At the end of the process,  $v_C = V_S$  and  $i = 0$ . This is steady state condition.

→ when the switch is in the lower position, the charge stored in the capacitor will flow through the resistor that will dissipate the energy as heat – this is transient state again until the capacitor is fully discharged. At the end of the process it will be steady state condition again, with  $v_C = 0$  and  $i = 0$ .

$$v_C(t) = V_{ss} - (V_{ss} - V_i)e^{-\frac{t}{\tau}}$$

$$\tau = RC$$

$\tau$  – time constant (s) – the larger  $R$  or  $C$  is, the longer it takes for the capacitor to charge up.

$$i_C(t) = I_{ss} - (I_{ss} - I_i)e^{-\frac{t}{\tau}}$$

$V_{ss}$  – steady state or final voltage across the capacitor after  $5\tau$ .

$V_i$  – initial voltage across the capacitor (V)

$I_{ss}$  – steady state or final current (A)

$I_i$  – initial current (A)


$t$  – time (s)

→ if the capacitor is fully discharged before the source voltage is applied, then  $V_i = 0$ :

$$v_C(t) = V_{SS} \left( 1 - e^{-\frac{t}{\tau}} \right)$$

→ when  $I_{SS} = 0$ :  $i_C(t) = I_i e^{-\frac{t}{\tau}}$   $I_i = \frac{V_S}{R}$

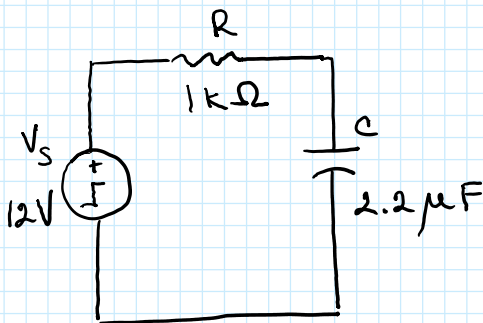Ex: Find the expression for capacitor voltage and current step response (capacitor fully discharged initially).





→ in a steady state, the capacitor acts like an open circuit in DC, and like a short circuit in AC.

DC, and like a short circuit in AC.




Ex: For the circuit below, calculate:

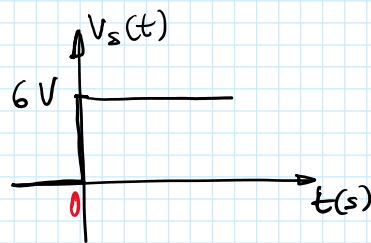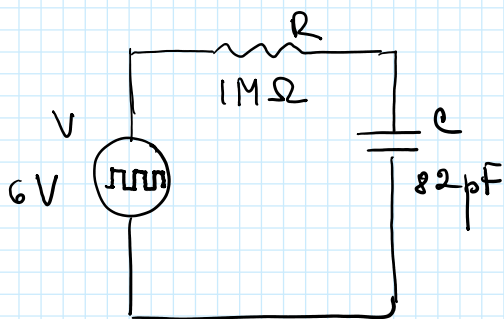- The current flowing in the circuit immediately after the source voltage switches from 0 to 6 V.
- The voltage across the capacitor when  $t = \tau$ .



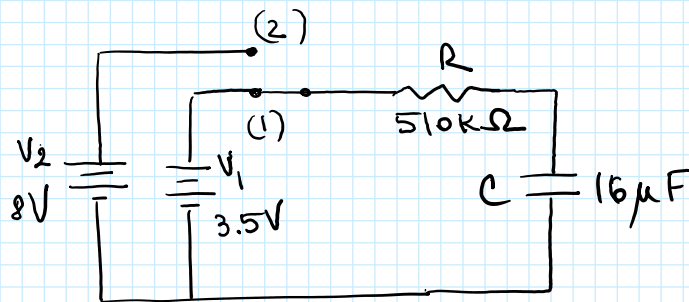
Ex: For the circuit below, assume that the switch moves from terminal 1 to terminal 2 at  $t=0$ . Calculate the voltage across the capacitor at  $t = 180 \mu s$ . Redo the calculations if the values of the voltages are switched.


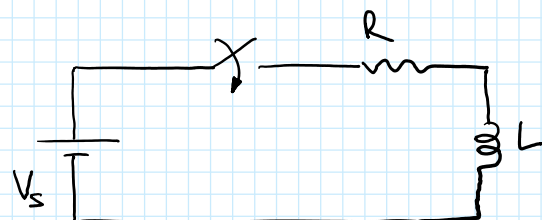
### Series RL Circuit Step Response

$$\tau = L/R$$

$$\begin{cases} v_L(t) = (I_{ss}R)e^{-\frac{t}{\tau}} = V_s e^{-\frac{t}{\tau}} \\ i_L(t) = I_{ss} - (I_{ss} - I_i)e^{-\frac{t}{\tau}} \end{cases}$$



$$I_{ss} = \frac{V_s}{R}$$

$$I_i = 0 \text{ (inductor fully discharged)}$$

Ex: For the circuit below, calculate the values of the inductor voltage and current after  $3 \mu s$ . Assume the inductor is fully discharged initially.

